
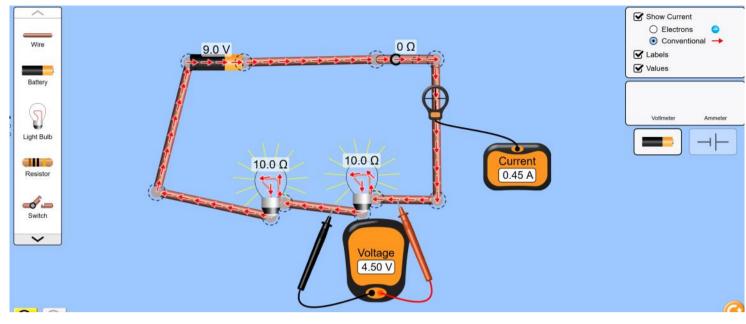
## Lesson 0 Voltage Solution

In series (which was by far the most common solution)



Screen clipping taken: 2020-04-14 2:32 PM
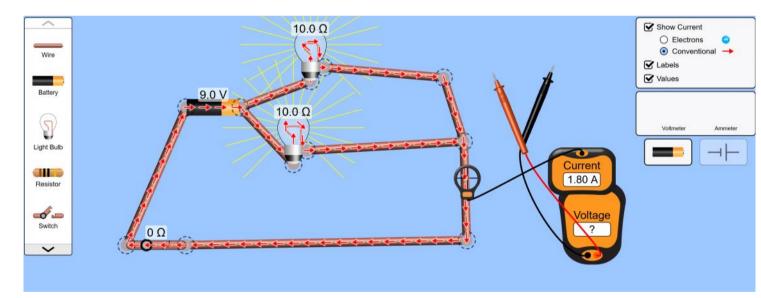
## In parallel (which most of you didn't think of)



Screen clipping taken: 2020-04-14 2:30 PM