
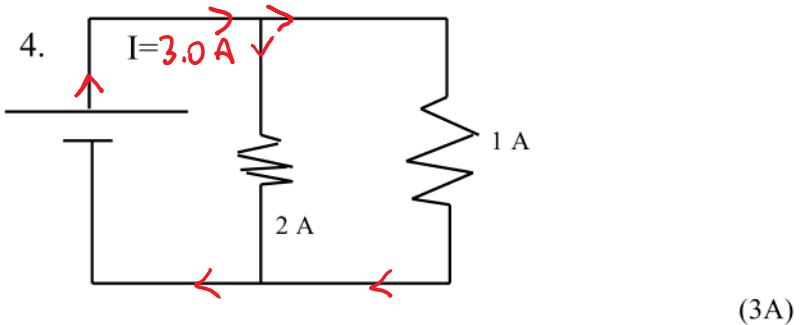
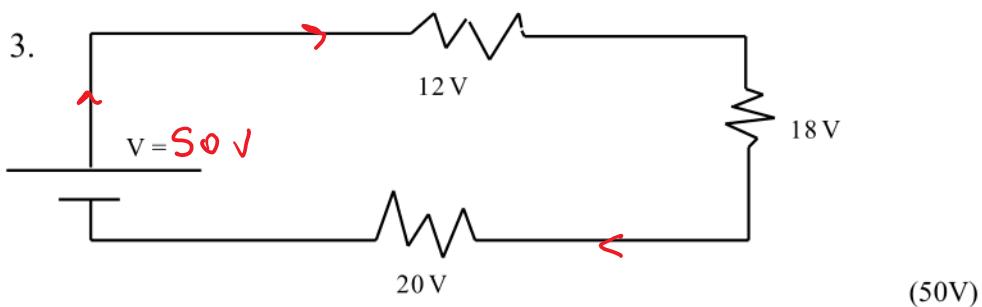
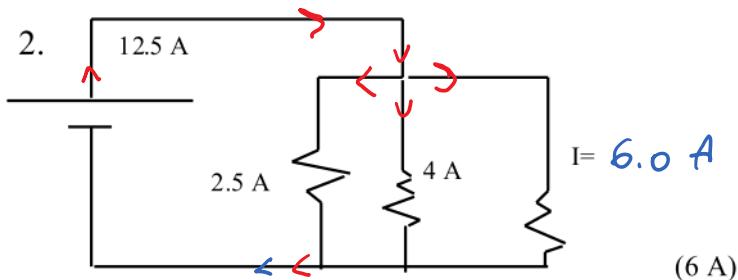


Lesson 3 Homework Solutions


May 5, 2020 7:28 PM

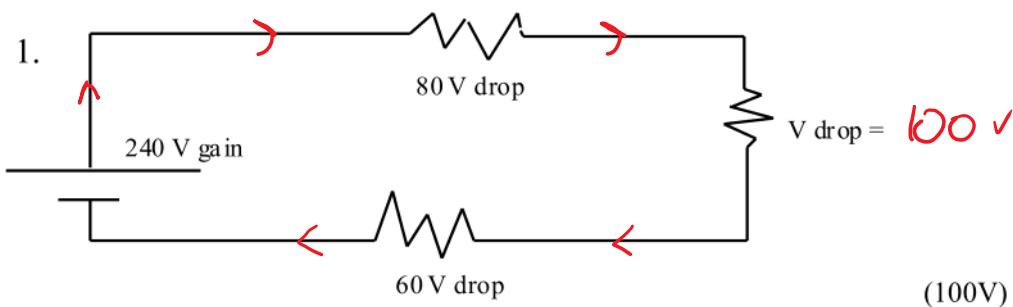exercises: find unknown voltages and currents



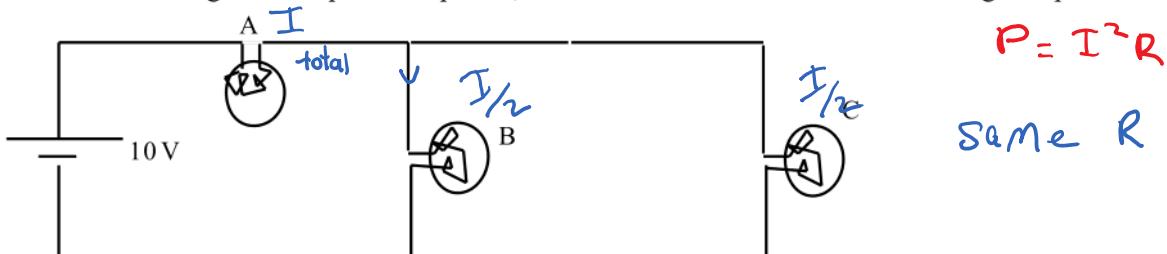5. The three bulbs below are identical- which bulb is brightest? Explain your answer. i) bulb A
B ii) bulb C iii) bulb C iv) equally bright


Note that bulb brightness depends on power, and therefore on both current and voltage drop



6. Find unknown voltages and currents


4 V

6. Find unknown voltages and currents

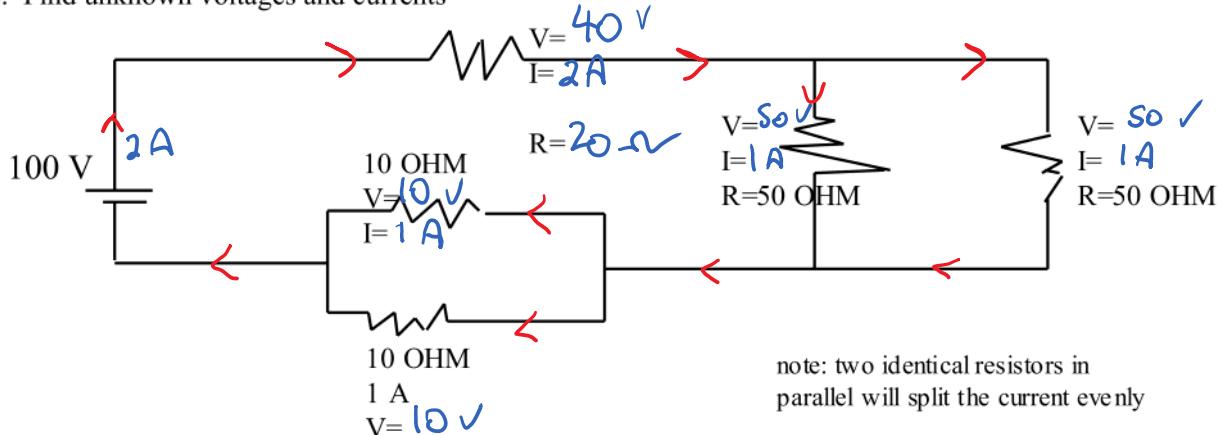


$$V = IR$$


7. Find unknown voltages and currents

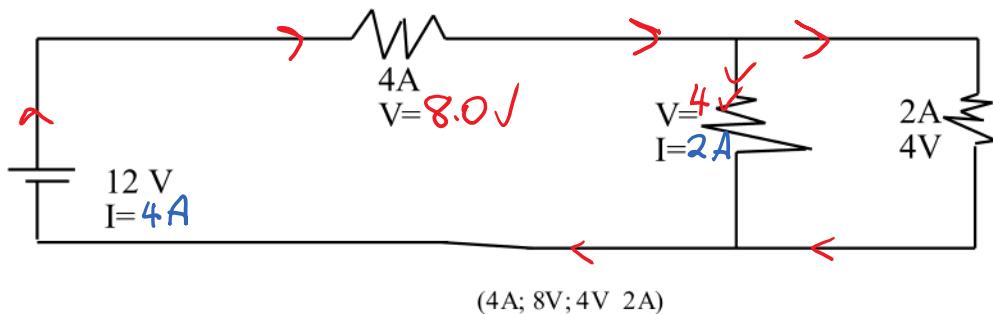


8. Find unknown voltages and currents

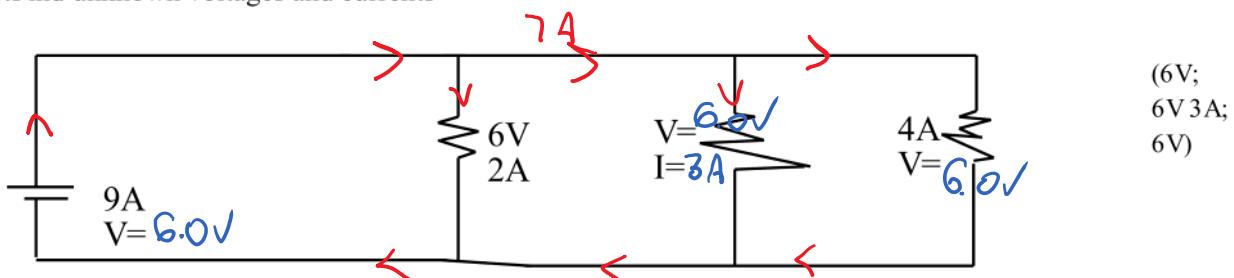


9. Find unknown voltages and currents

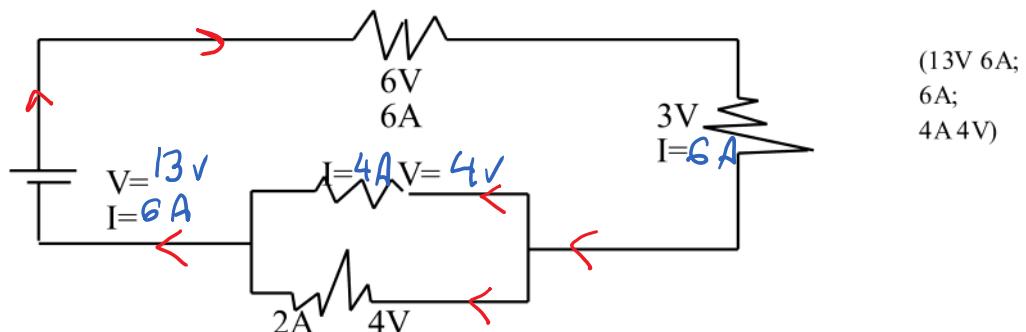


10. Find unknown voltages and currents

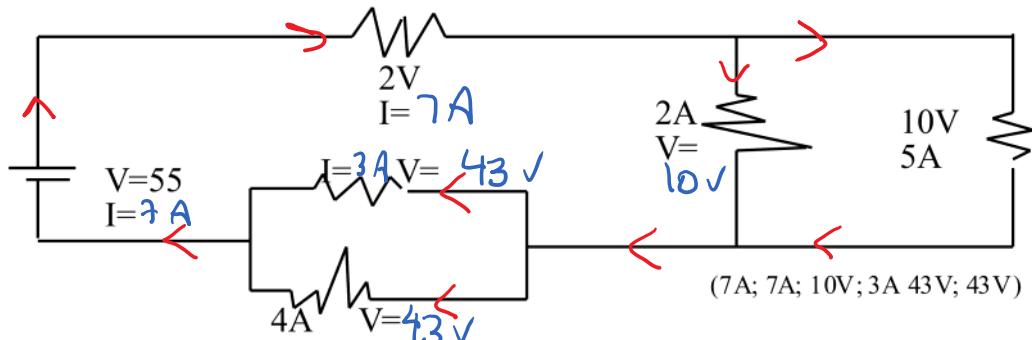


11. Find unknown voltages and currents

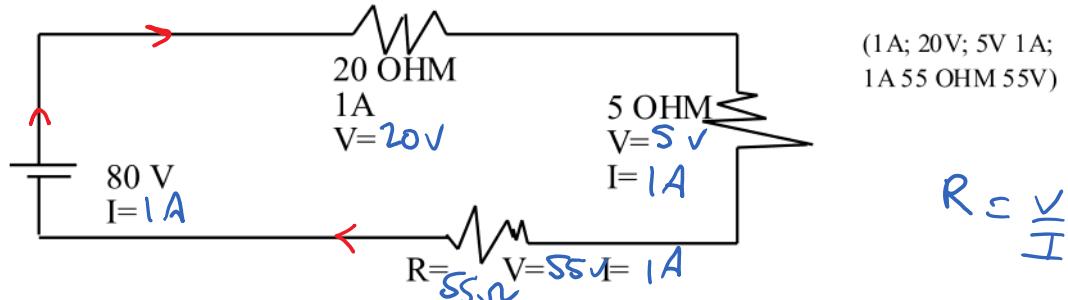


12. Find unknown voltages and currents

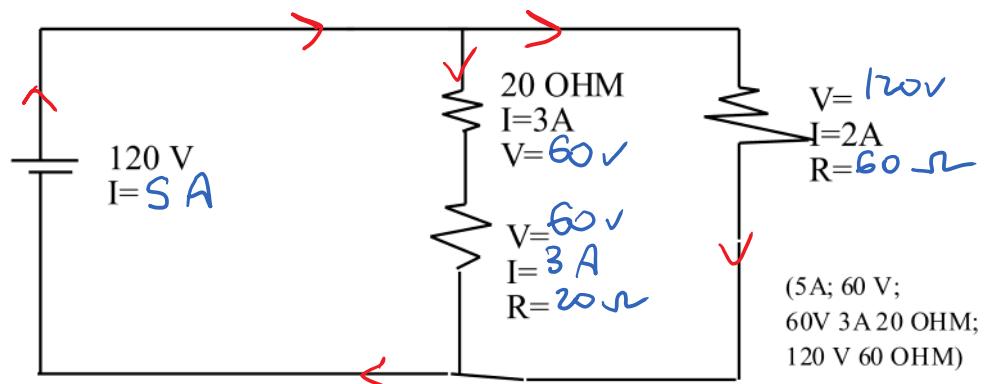


13. Find unknown voltages and currents

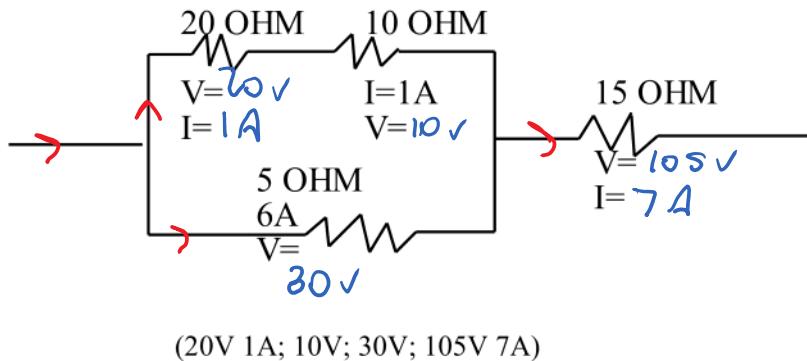

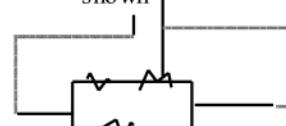note: in problems such as these, assume that the two end wires are connected to a cell that has not been shown




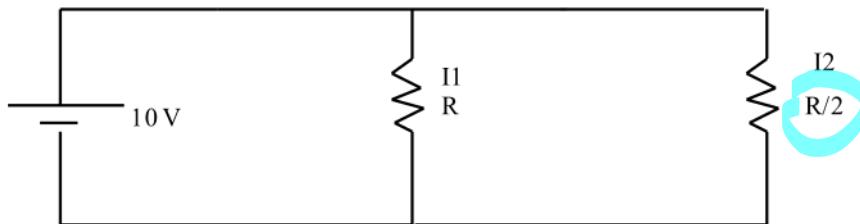14. What can be said about the currents I_1 and I_2 if the resistance of R_2 is half the resistance of R_1 ?




$$I_2 = 2 * I_1$$

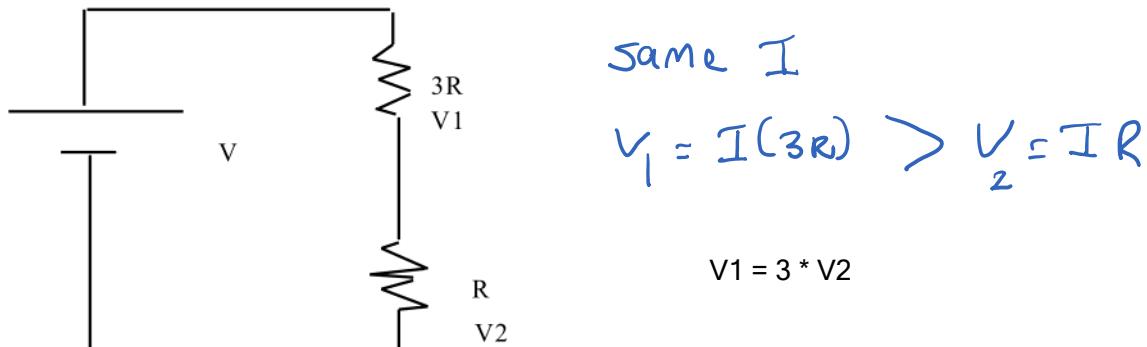15. What can be said about the voltage drops V_1 and V_2 if the resistance of R_1 is three times the resistance of R_2 ?



explain your answer using appropriate physics principles

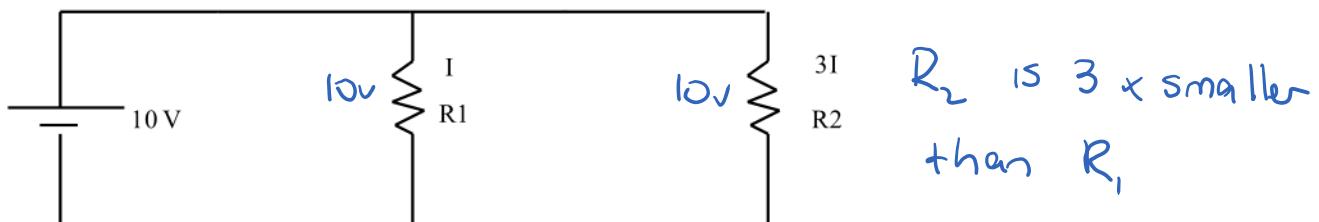16. What can be said about the resistances R_1 and R_2 if the current through R_2 is three times the current through R_1 ?



explain your answer using appropriate physics principles

$$R = \frac{V}{I}$$