
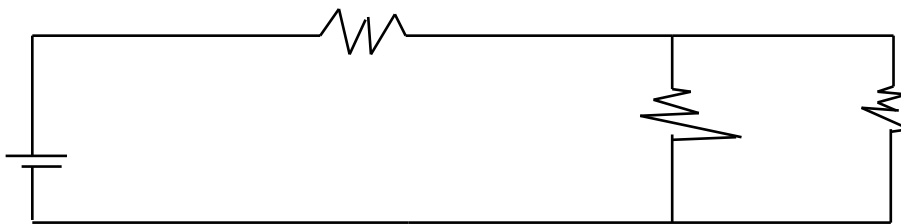



Lesson 4: Series and Parallel Circuits

• a series circuit is a circuit where resistors are connected in a row with no junctions in between them

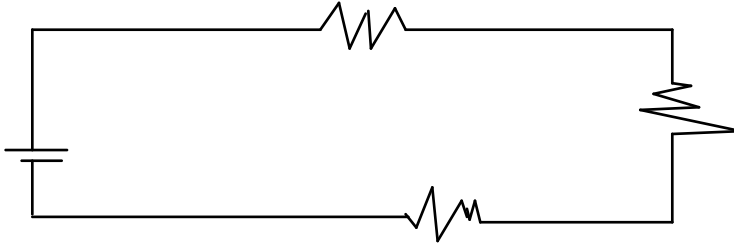• example 1: which circuits show resistors in (simple) series?



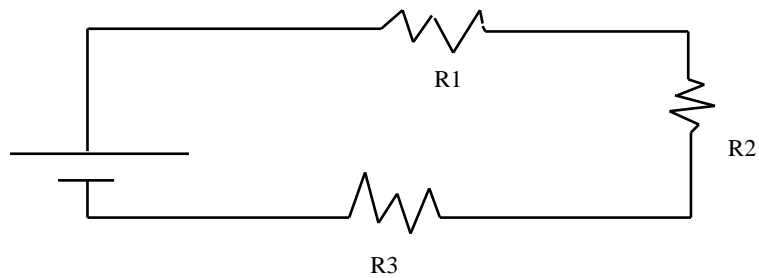• example 2: find an expression for the total resistance of a series circuit



KVL says:

KCL says:

total resistance $R_t =$

=


=

=

series $R_t =$

$$R = \Omega = \text{ohm}$$

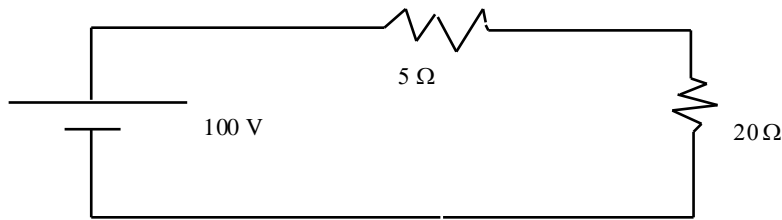
•example 3: Select the best answer for the voltage drop across the 20Ω resistor



- a) 100 volts
- b) more than 50 volts
- c) less than 50 volts



explain your answer using relevant physics principles

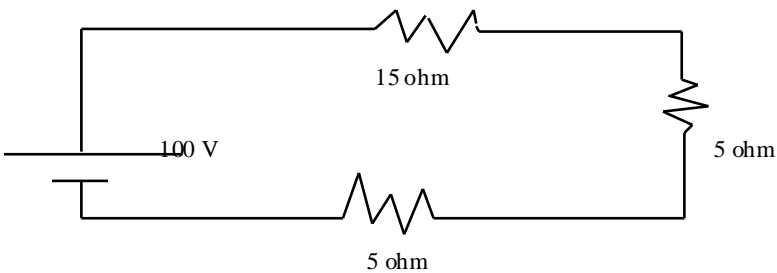•example 4: find total resistance and current, then find the current through and voltage drop across each resistor




•a parallel circuit is a circuit where resistors start and end at the same voltage (height)...i.e. the resistors are directly connected at the top and at the bottom with no other resistors in between

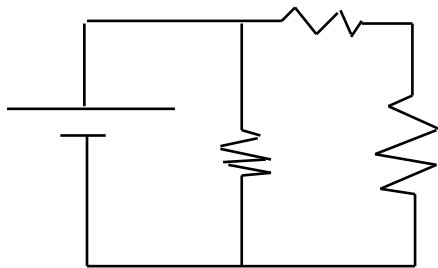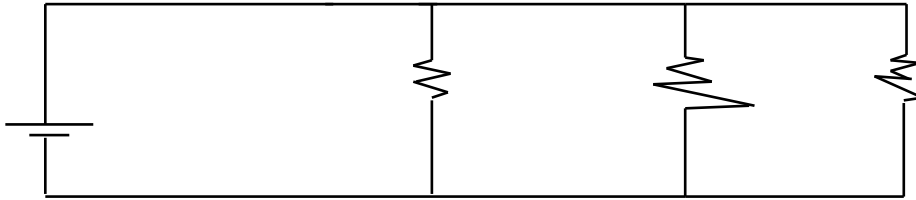•example 5: which circuit shows resistors in (simple) parallel?



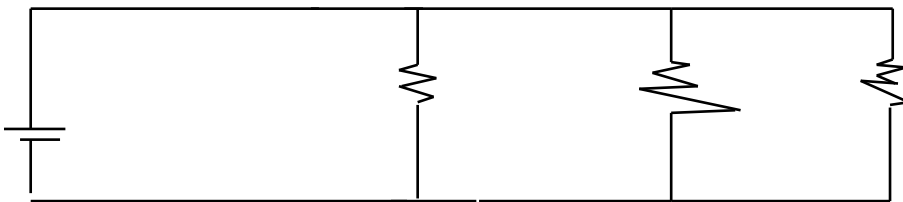•example 6: find an expression for the total resistance of a parallel circuit



KVL says:

KCL says:

total resistance $\frac{1}{R_t} =$

=


=

=


parallel $R_t =$

$R = \Omega = \text{ohm}$

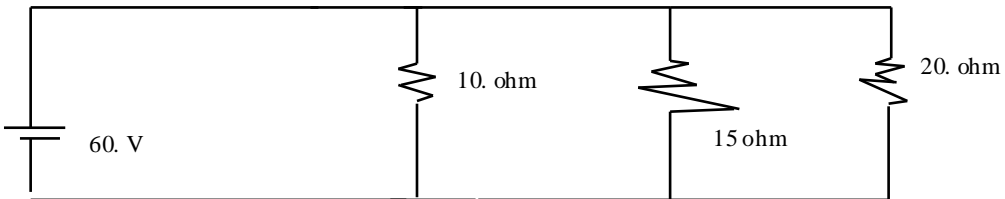•example 7: find R_t and I_t , then find V, I for all resistors



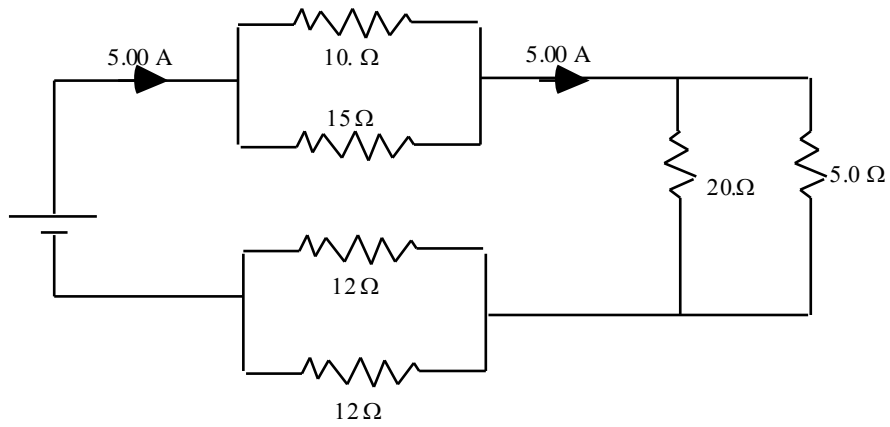
•example 8: Find the voltage and power lost in each resistor, and then find the voltage of the battery.



• example 8 illustrates an important point. It shows us that the voltage drop across parallel resistors is the same as the drop across the equivalent resistor in the equivalent circuit.


•In a household circuit, plugs and lights are wired in parallel to 120 volts AC. Each circuit has a circuit breaker in the circuit. The circuit breaker is an automatic switch that opens when the current exceeds a set value(15 Amp usually). When the switch is opened, no more current flows through the circuit.

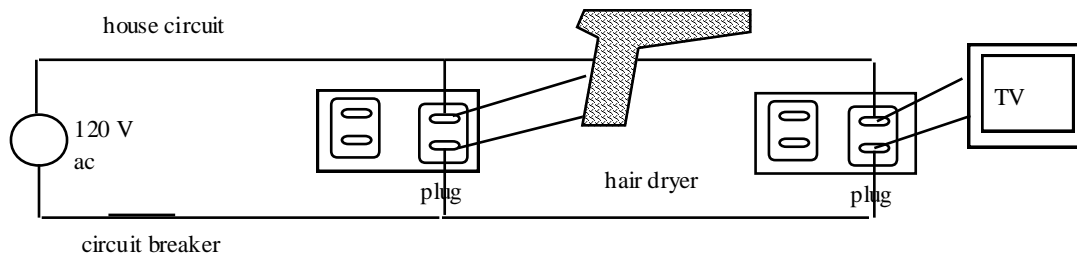•example 9: If we connect a 1200 Watt hairdryer and a 500 Watt TV to the same circuit, will we cause the 15 A breaker to trip?




Exercises

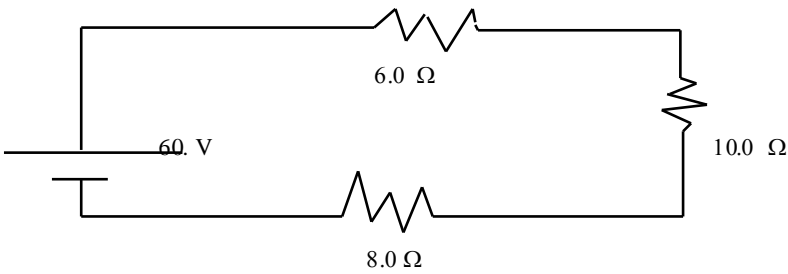1. Find all unknown voltages and currents (2.5 A, 15V; 2.5A, 25V; 2.5 A, 20. V)




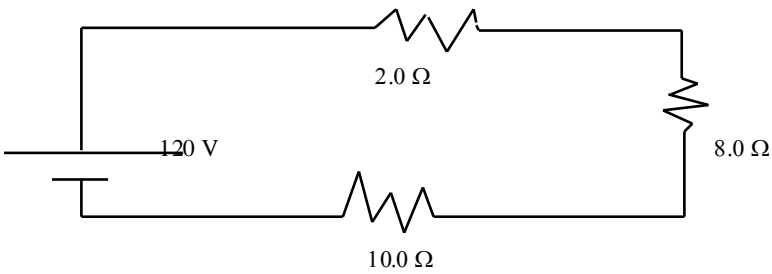2. Find all unknown voltages and currents (6.0 A, 12 V; 6.0 A, 48 V; 6.0 A, 60. V)




3. Find all unknown voltages, currents and resistances

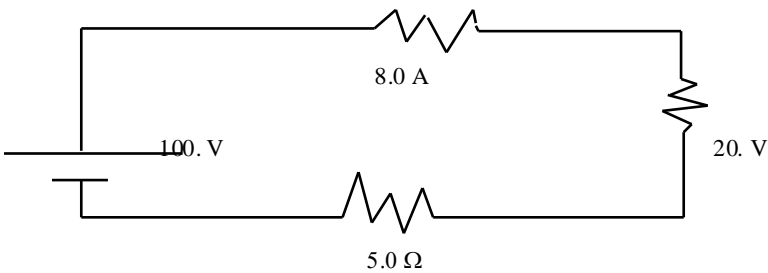(5.0 Ω, 40. V; 8.0 A, 2.5 Ω; 8.0 A, 40 V)




4. Which resistors are in series?

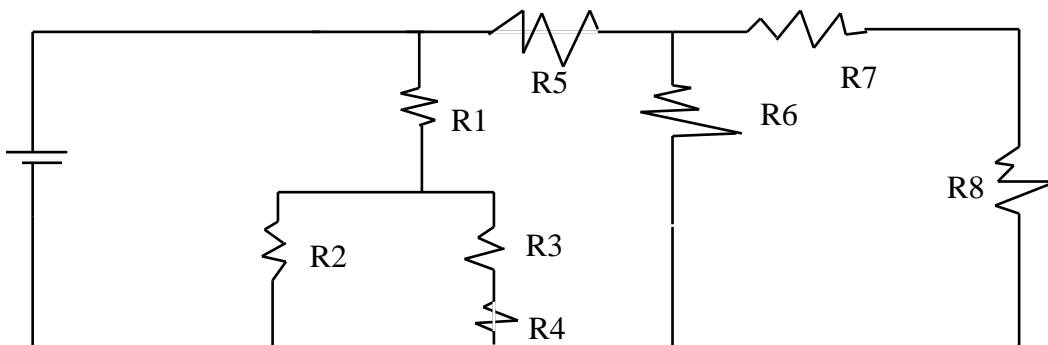

Ans: (R7 and R8), (R3 and R4)

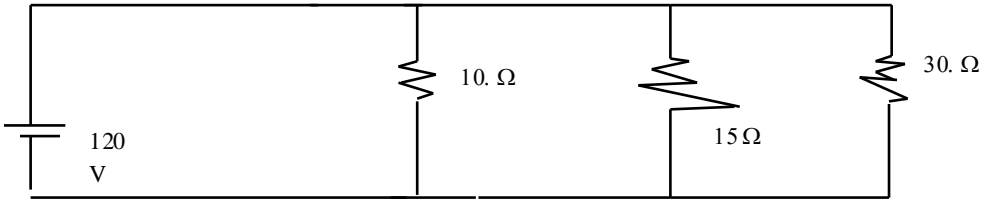
6. Find all voltage drops and currents (120 V, 12A; 120V,8.0A;120V,4.0A)



7. Find the total current in #6 if we

- a) remove the 15 ohm (16A)
- b) remove the 30. ohm (20. A)
- c) add another 10. ohm in parallel (36 A)
- d) add a 120 ohm in parallel (25 A)

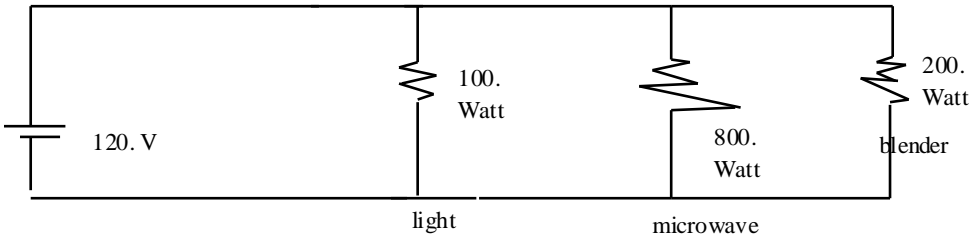8. Find all voltage drops and currents (120. V,0.833 A;120.V, 6.67 A; 120. V,1.67 A)




9. i) In household circuit #8, find the total current if we make the following changes to the circuit.
- ii) Indicate (yes or no) if these changes would cause the circuit breaker to trip (this happens when the total current exceeds 15.0 A)
- a) adding another 100. W light (in parallel) (no, $I_t=10.0$ A)
 - b) removing the 800. W microwave (no $I_t=2.50$ A)
 - c) adding a 1400. W hair dryer (in parallel) (yes $I_t= 20.8$ A)
 - d) adding a 300. W computer (in parallel) (no $I_t = 11.7$ A)

10. What is the maximum number of the following in a house circuit (note: an outlet has $V=120$ V, and max current is 15 A)

- a) 100 W light bulbs
- b) 250 W TV's
- b) 10 W toothbrushes
- d) 800 W toasters

(18; 7;180; 2)

11. Which resistors are in parallel?

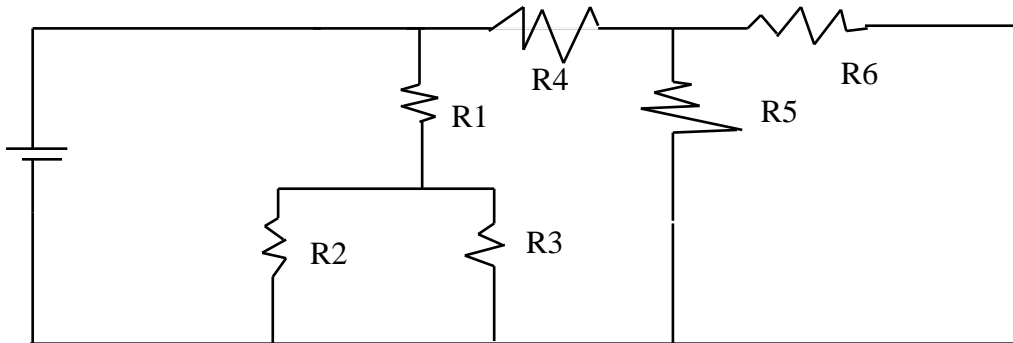


Ans: (R1 and R4), (R2 and R3), (R5 and R6)

14. If we add a resistor in parallel to a parallel circuit, what happens to the total resistance?

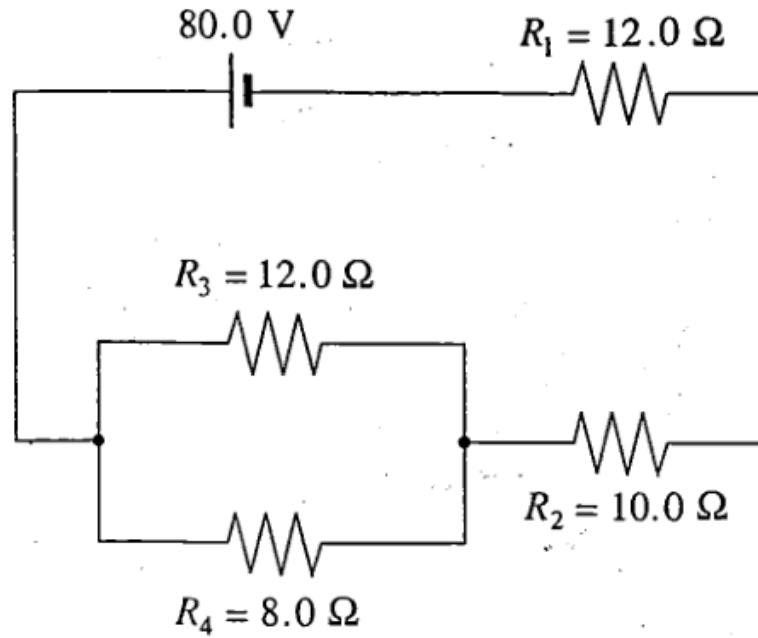- a) it increases
- b) it decreases
- c) it may increase or decrease depending on the value of the resistance we add.

Ans: (b) Bonus: Can you prove it?

What is the power dissipated in the $8.0\ \Omega$ resistor in the circuit as shown?



Ans: 26 W