

Unit 7 Quiz 1 Answers

May 13, 2020 9:26 PM

Physics 12


Score: ____/16

Name: Anne Surkee

Unit 7 Quiz 1 Version 1

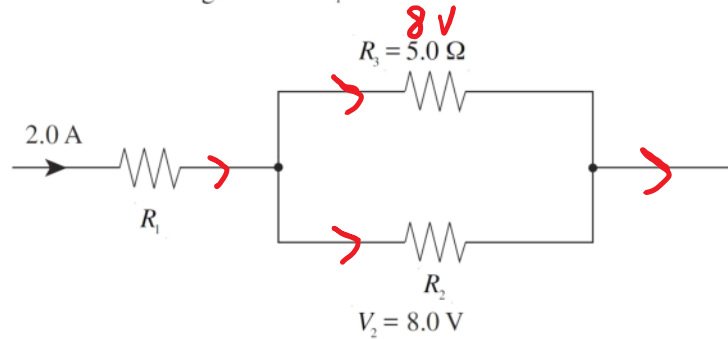1.

A current of 2.0 A flows through resistor R_1 as shown below.




What is the current flowing through the 5.0Ω resistor?

- A. 0.40 A
- B. 1.0 A
- C. 1.2 A
- D. 1.6 A

$$I = \frac{V}{R} = \frac{8}{5}$$

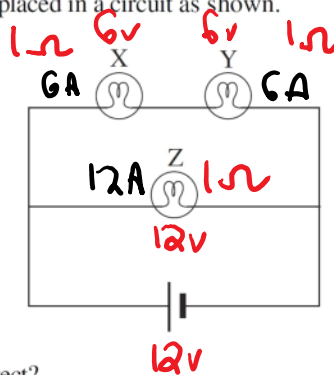
2. Three identical light bulbs are placed in a circuit as shown.



Which of the following is correct?

- A. The voltage and current are the same for all three bulbs.
- B. The current in light bulb Z is less than the current in light bulb X.
- C. The current in light bulb Z is greater than the current in light bulb Y.
- D. The voltage across light bulb Z is less than the voltage across light bulb X.

3.

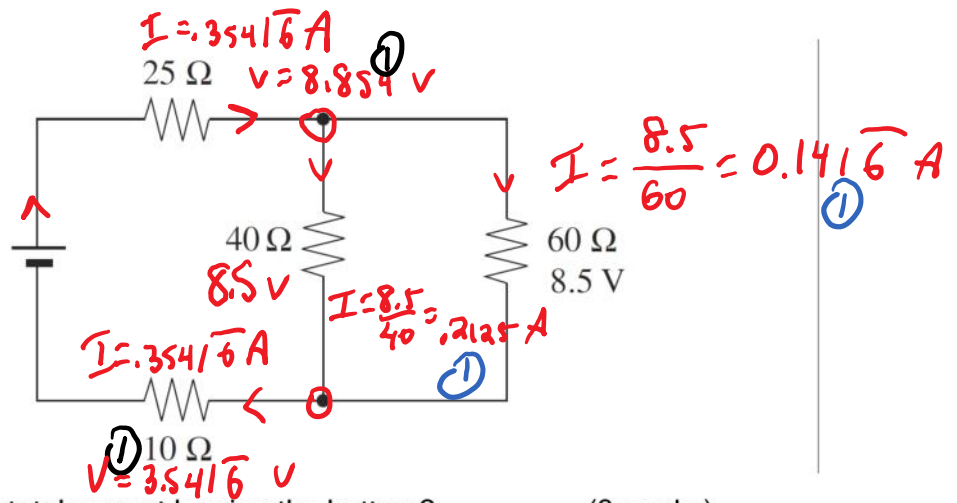

a) What is the total current leaving the battery? (3 marks)

$$I_T = 0.1416 + 0.2125 = 0.35416 \text{ A}$$


(Each term and the result are marked with a circled 1)

b) What is the voltage of the battery? (4 marks)

$$V_{\text{total}} = 8.854 + 8.5 + 3.5416 = 20.9 \text{ V}$$

(Each term and the result are marked with a circled 1. The result is boxed in red)

4.

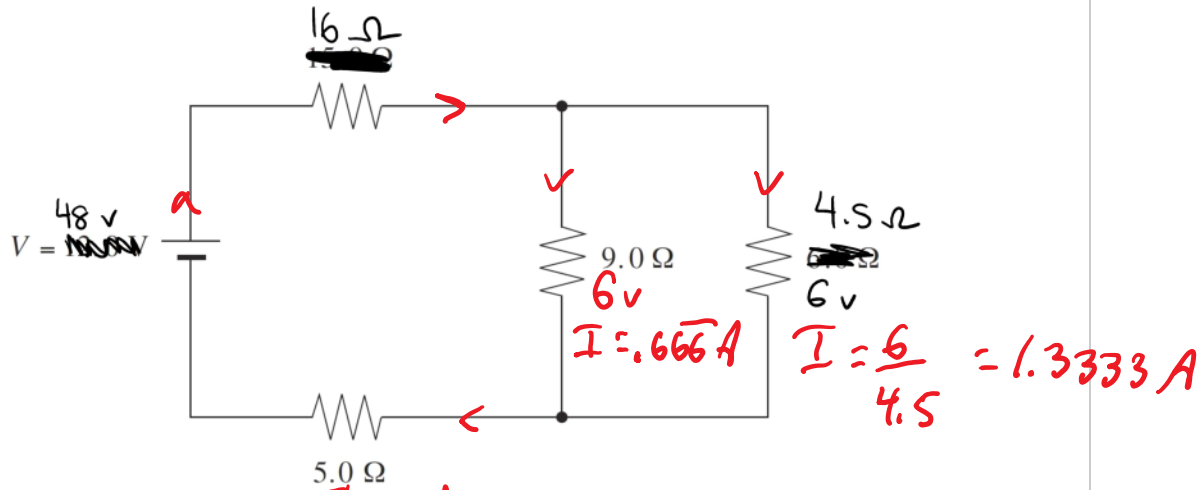

a) Find the power loss through the $5\ \Omega$ resistor. (4 marks)

$$I_T = 0.666 + 1.333 = 2.0\text{ A}$$

$$P = I^2 R = 2^2 (5) = 20\text{ W}$$

b) Suppose the $4.5\ \Omega$ resistor is removed from the circuit. If the $5\ \Omega$ resistor is a light bulb, how does its brightness compare to its brightness in part (a)?

The bulb is: brighter dimmer unchanged

(circle the correct answer) (1 mark)

c) Using principles of physics, defend your answer to part (b) (2 marks)

Remove resistor in parallel: $R_T \uparrow$ (to $30\ \Omega$)

If $R_T \uparrow$, then $I_T \downarrow$ ($I_T = \frac{V_T}{R_T} = 1.6\text{ A}$)

Since $P = I_T^2 R$, power in the $5\ \Omega$ will be smaller, so dimmer